

Uvod u teoriju linija

el. krugovi s koncentriranim elementima

→ d. svojstva ne ovise o ugrađenim fiz. dimenzijama

→ trenutni odziv u svakoj drugoj točki mreže


Na vrlo visokim frekv → valna dužina signala može postati usporediva s

• nema trenutnog odziva na promjenu poluge fiz. dimenzijama

Električne prijenosne linije

* par paralelnih vodiča

→ idealizirani model linije:

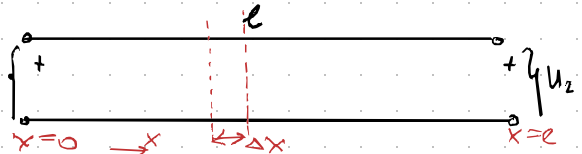

▷ liniji nije moguće prikazati koncentriranim elementima R, L, C , a ko
myena dužina nije puno kraća od najmanje valne dužine signala koji
prijenosi

R → otpor linije po jedinici dužine [Ω/m]


L → induktivitet [H/m]

G → vodljivost [S/m]


C → kapacitet [F/m]

Zamislamo
jedan segment
linije Δx

→ na njemu
mijene konc.
parametri

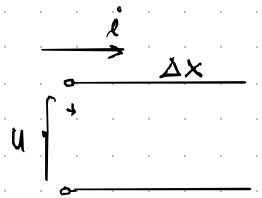

⇒ to onda izgleda ovako:

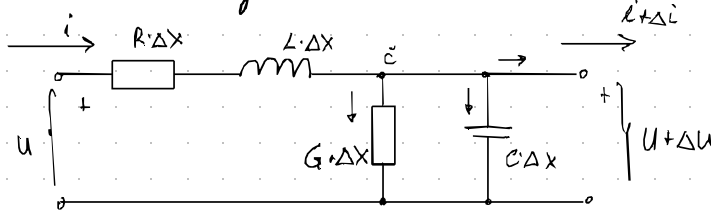

Linija koje promatramo:

→ LINEARNE
(ne ovise o $u(x,t)$ i $i(x,t)$)

→ VREMENSKI NEPROM. (neovisno o vremenu)

→ HOMOGENE
(ne ovise o mjestu x)

jednadžbe:

$$u = (R \cdot \Delta x) i + (L \Delta x) \frac{di}{dt} + u + \Delta u$$

$$i = (G \cdot \Delta x)(u + \Delta u) + (C \cdot \Delta x) \frac{d(u + \Delta u)}{dt} + i + \Delta i \Rightarrow 0 = G \Delta x u + G \Delta x \Delta u + C \Delta x \frac{du}{dt} + C \Delta x \frac{d\Delta u}{dt} + \Delta i$$

$$\hookrightarrow 0 = (R \Delta x) i + L \Delta x \frac{di}{dt} + \Delta u$$

$$0 = G \Delta x \cdot u + C \Delta x \frac{du}{dt} + \Delta i \quad / \cdot \Delta x$$

$$-\frac{\Delta u}{\Delta x} = R i + L \frac{di}{dt}$$

albo ne Δx smanjuje t.d. $\Delta x \rightarrow 0$

$$-\frac{\Delta i}{\Delta x} = G u + C \frac{du}{dt}$$

$$\Rightarrow \begin{cases} -\frac{\partial u}{\partial x} = R i + L \frac{\partial i}{\partial t} \\ -\frac{\partial i}{\partial x} = G u + C \frac{\partial u}{\partial t} \end{cases} \Rightarrow \text{jednadžbe linija}$$

$$* u = u(x, t)$$

$$i = i(x, t)$$

↓
zavisne nezavisne var.

Dif. jed. moguće transform. u drugi oblik

$$\frac{\partial u(x,t)}{\partial x} + Ri + L \frac{\partial i(x,t)}{\partial t} = 0 \quad \bigg/ \quad \frac{\partial}{\partial t} \quad \boxed{-\frac{\partial^2 u}{\partial x \partial t}} = R \cdot \frac{\partial i}{\partial t} + L \frac{\partial^2 i}{\partial t^2}$$


$$\frac{\partial i(x,t)}{\partial x} + Gu + C \cdot \frac{\partial u(x,t)}{\partial t} = 0 \quad \bigg/ \quad \frac{\partial}{\partial x} \quad \Rightarrow \quad -\frac{\partial^2 i}{\partial x^2} = G \cdot \frac{\partial u}{\partial x} + C \cdot \frac{\partial^2 u}{\partial t \partial x}$$

$$\Rightarrow \frac{\partial^2 i(x,t)}{\partial x^2} = LC \frac{\partial^2 i(x,t)}{\partial t^2} + (LG + RC) \frac{\partial i(x,t)}{\partial t} + R \cdot G \cdot i(x,t) \rightarrow \text{dif. jed. za struju}$$

$$\Rightarrow \frac{\partial^2 u(x,t)}{\partial x^2} = LC \frac{\partial^2 u(x,t)}{\partial t^2} + (RC + LG) \frac{\partial u(x,t)}{\partial t} + R \cdot G \cdot u(x,t) \rightarrow \text{dif. jed. za napon}$$

L telegrafске jednačine linije

Primer:

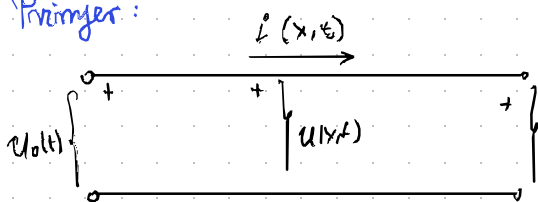

→ određiti napon i struju na bilo kojem mestu x linije

• rješava dif. jed. → Laplaceove trans.

$$\begin{aligned} -\frac{\partial u}{\partial x} &= R \cdot i + L \frac{\partial i}{\partial t} \\ -\frac{\partial i}{\partial x} &= G \cdot u + C \cdot \frac{\partial u}{\partial t} \end{aligned} \quad \xrightarrow{\mathcal{L}} \quad \begin{aligned} -\frac{\partial U(x,s)}{\partial x} &= R \cdot I(x,s) + Ls \cdot I(x,s) - i(x,0) \\ -\frac{\partial I(x,s)}{\partial x} &= G \cdot U(x,s) + Cs \cdot U(x,s) - u(x,0) \end{aligned}$$

$$-\frac{\partial U}{\partial x} = R \cdot I(x,s) + L(s \cdot I(x,s) - i(x,0)) \quad \text{u vremenu } t=0 \quad \text{— pretpostavka } u(x,0) \text{ i } i(x,0)=0$$

$$-\frac{\partial I(x,s)}{\partial x} = G \cdot U(x,s) + C(s \cdot U(x,s) - u(x,0))$$

$$-\frac{\partial U}{\partial x} = (R + Ls) I(x,s) \quad \bigg/ \quad \frac{\partial}{\partial x} \quad \rightarrow \quad -\frac{\partial^2 U}{\partial x^2} = (R + Ls) \frac{\partial I(x,s)}{\partial x}$$

$$-\frac{\partial I}{\partial x} = (G + Cs) U(x,s) \quad \Rightarrow \quad \frac{\partial^2 U}{\partial x^2} = (R + Ls)(G + Cs) U(x,s)$$

$$\dots \text{ isto tako i struju: } \frac{\partial^2 I}{\partial x^2} = (R + Ls)(G + Cs) I(x,s)$$

$$\frac{\partial^2 U}{\partial x^2} - \gamma^2 U(x,s) = 0 \rightarrow \text{HJ 2. reda za raspodelu napona duž linije}$$

$$\frac{\partial^2 I}{\partial x^2} - \gamma^2 I(x,s) = 0 \rightarrow \text{HJ 2. reda za raspodelu struje duž linije}$$

Opće rješenje za napon → eksp. oblika $U(x,s) = Ae^{\gamma x}$

$$\Rightarrow A\gamma^2 e^{\gamma x} - \gamma^2 A e^{\gamma x} = 0 \quad \bigg/ \quad A e^{\gamma x}$$

$$\gamma^2 - \gamma^2 = 0 \rightarrow \gamma_{1,2} = \pm \gamma \quad \text{jednakostranični jed.}$$

Dif. jed. za raspodelu napona

$$U(x,s) = A_1 e^{-\gamma x} + A_2 e^{\gamma x}$$

γ = faktor prenosa $\gamma(s) = \sqrt{(R + Ls)(G + Cs)}$ ≠ 0 i s 0 ≠ faktor propagacije

RJ. Dif. jed. za raspodelu struje

$$I(x,s) = B_1 e^{-\gamma x} + B_2 e^{\gamma x}$$

Konstante se određuju iz rubnih uslova

$$r.u. \Rightarrow U(0,s) \quad I(0,s) \quad U(l,s) \quad I(l,s)$$

Uvrštenjem rješenja za $U(x,s)$ i $I(x,s)$ dobiva se

$$A_1 \underline{e^{-\gamma x}} - A_2 \gamma \underline{e^{\gamma x}} = (R+SL)(B_1 \underline{e^{-\gamma x}} + B_2 \underline{e^{\gamma x}})$$

$$\underline{e^{-\gamma x}} (A_1 \gamma + (R+SL) B_1) - \underline{e^{\gamma x}} (A_2 \gamma + (R+SL) B_2) = 0 \quad / : \gamma$$

$$\underline{e^{-\gamma x}} \left(A_1 + \frac{R+SL}{\gamma} B_1 \right) - \underline{e^{\gamma x}} \left(A_2 + \frac{R+SL}{\gamma} B_2 \right) = 0$$

$$\downarrow = \sqrt{\frac{R+SL}{G+SC}} = Z_0 \quad \text{valna ili karakt. impedancija linije}$$

$$\Rightarrow A_1 - Z_0 B_1 = 0 \rightarrow B_1 = \frac{A_1}{Z_0}$$

$$A_2 + Z_0 B_2 = 0 \rightarrow B_2 = -\frac{A_2}{Z_0}$$

$$U(x,s) = A_1 \underline{e^{-\gamma x}} + A_2 \underline{e^{\gamma x}}$$

$$I(x,s) = \frac{A_1}{Z_0} \underline{e^{-\gamma x}} - \frac{A_2}{Z_0} \underline{e^{\gamma x}}$$

• Rubni uvjeti za $x=0 \rightarrow U(0,s) = U(0)$
 $I(0,s) = I(0)$

$$U(0) = A_1 \underline{e^{-\gamma \cdot 0}} + A_2 \underline{e^{\gamma \cdot 0}} = A_1 + A_2$$

$$I(0) = \frac{A_1}{Z_0} - \frac{A_2}{Z_0}$$

$$\Rightarrow \underline{A_1 = \frac{U(0) + I(0) \cdot Z_0}{2}}$$

$$\underline{A_2 = \frac{U(0) - I(0) \cdot Z_0}{2}}$$

Rješenje za napon i struju na mjestu x
 liniji:

$$U(x,s) = \frac{U(0) + I(0) \cdot Z_0}{2} \underline{e^{-\gamma x}} + \frac{U(0) - I(0) \cdot Z_0}{2} \underline{e^{\gamma x}}$$

$$I(x,s) = \frac{\frac{U_0}{Z_0} + I(0)}{2} \underline{e^{-\gamma x}} - \frac{\frac{U_0}{Z_0} - I(0)}{2} \underline{e^{\gamma x}}$$

→ Drugi oblik $\Rightarrow \text{ch}(\gamma x)$ \uparrow sh(γx)

$$U(x) = U(0) \frac{e^{\gamma x} + e^{-\gamma x}}{2} - Z_0 I(0) \frac{e^{\gamma x} - e^{-\gamma x}}{2}$$

$$I(x) = -\frac{U_0}{Z_0} \frac{e^{\gamma x} - e^{-\gamma x}}{2} + I(0) \frac{e^{\gamma x} + e^{-\gamma x}}{2}$$

$$U(x) = U(0) \text{ch}(\gamma x) - Z_0 I(0) \text{sh}(\gamma x)$$

$$I(x) = -\frac{U(0)}{Z_0} \text{sh}(\gamma x) + I(0) \text{ch}(\gamma x)$$

$$U(0) = U(x) \cdot \text{ch}(\gamma x) + Z_0 I(x) \text{sh}(\gamma x)$$

$$I(0) = \frac{U(x)}{Z_0} \text{sh}(\gamma x) + I(x) \cdot \text{ch}(\gamma x)$$

Priglasne jednadžbe linije

- Linija je četvorpol

→ priglasni parametri

za $x=l$

$$U(0) = U(l) \operatorname{ch}(\gamma l) + Z_0 I(l) \cdot \operatorname{sh}(\gamma l)$$


$$I(0) = \frac{U(l)}{Z_0} \operatorname{sh}(\gamma l) + I(l) \operatorname{ch}(\gamma l)$$

→ priglasne jed. linije

Znači linija je simetričan četvorpol

$$A = \operatorname{ch}(\gamma l) = D \quad B = Z_0 \operatorname{sh}(\gamma l) \quad C = \frac{\operatorname{ch}(\gamma l)}{Z_0}$$

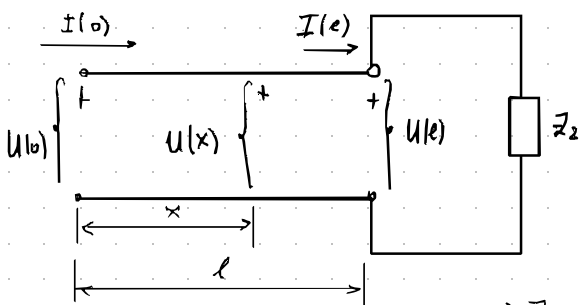Homogena linija zaključena impedancijom Z_2



za $x=l \rightarrow Z_2 = \frac{U(l)}{I(l)}$

$$U(l) = A_1 e^{-\gamma l} + A_2 e^{\gamma l}$$

$$I(l) = \frac{1}{Z_0} (A_1 e^{-\gamma l} - A_2 e^{\gamma l})$$

$$\Rightarrow Z_2 = \frac{U(l)}{I(l)} = Z_0 \cdot \frac{A_1 e^{-\gamma l} + A_2 e^{\gamma l}}{A_1 e^{-\gamma l} - A_2 e^{\gamma l}}$$

$$U(l) = A_1 e^{-\gamma l} + A_2 e^{\gamma l}$$

$$Z_0 I(l) = A_1 e^{-\gamma l} - A_2 e^{\gamma l} \Rightarrow$$

$$A_1 = \frac{1}{2} (U(l) + Z_0 I(l)) e^{\gamma l} \rightarrow A_1 = \frac{I(l)}{2} (Z_2 + Z_0) e^{\gamma l}$$

$$A_2 = \frac{1}{2} (U(l) - Z_0 I(l)) e^{-\gamma l} \rightarrow A_2 = \frac{I(l)}{2} (Z_2 - Z_0) e^{-\gamma l}$$

$$\Rightarrow \frac{A_2}{A_1} = \frac{Z_2 - Z_0}{Z_2 + Z_0} e^{-2\gamma l}$$

koefficient refleksije na izlazu

$$\Gamma_2 = \frac{Z_2 - Z_0}{Z_2 + Z_0}$$

$$A_2 = A_1 \Gamma_2 e^{-2\gamma l}$$

• napon na početku linije $x=0$

$$U(0) = A_1 + A_2 = A_1 (1 + \Gamma_2 e^{-2\gamma l}) \rightarrow$$

$$A_1 = \frac{U(0)}{1 + \Gamma_2 e^{-2\gamma l}}$$

$$A_2 = \frac{\Gamma_2 e^{-2\gamma l}}{1 + \Gamma_2 e^{-2\gamma l}} U(0)$$

• ako je poznat napon na početku lin.

onda napon i struja linije na bilo kom mjestu x linije:


$$U(x, s) = \frac{U(0)}{1 + \Gamma_2 e^{-2\gamma l}} (e^{-\gamma x} + \Gamma_2 e^{-2\gamma l} e^{\gamma x})$$

$$U(x, s) = U(0, s) \frac{e^{-\gamma(x-l)} + \Gamma_2 e^{\gamma(x-l)}}{e^{-\gamma l} + \Gamma_2 e^{\gamma l}}$$

$$I(x, s) = \frac{U(0)}{Z_0 (1 + \Gamma_2 e^{-2\gamma l})} (e^{-\gamma x} + \Gamma_2 e^{-2\gamma l} e^{\gamma x})$$

$$I(x, s) = \frac{U(0, s)}{Z_0} \frac{e^{-\gamma(x-l)} - \Gamma_2 e^{\gamma(x-l)}}{e^{-\gamma l} + \Gamma_2 e^{\gamma l}}$$

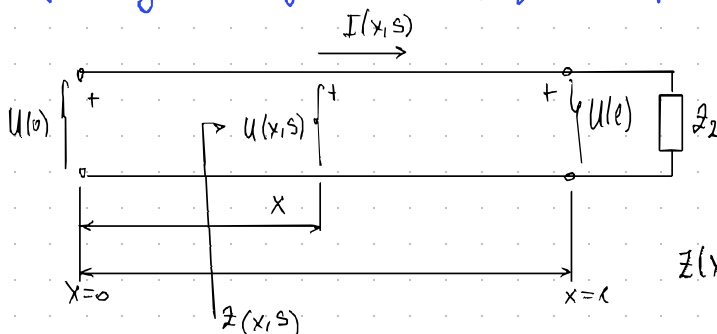
► Impedancija na mjestu x linije gledana prema izlazu



$$Z(x, s) = \frac{U(x, s)}{I(x, s)}$$

$$Z(x, s) = Z_0 \frac{e^{-\gamma(x-l)} + \Gamma_2 e^{\gamma(x-l)}}{e^{-\gamma(x-l)} - \Gamma_2 e^{\gamma(x-l)}}$$

Linija zaključena na oba kraja

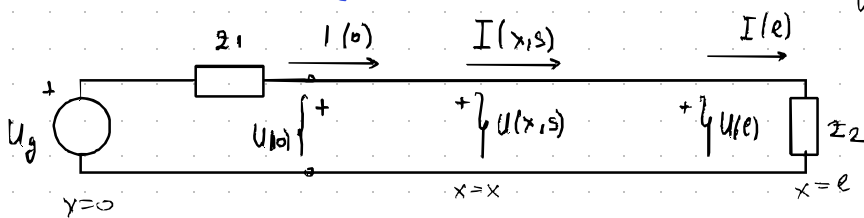

$$U(0) = U_g - Z_1 I(0)$$

$$U(l) = I(l) \cdot Z_2$$

$$U(0) = A_1 + A_2$$

$$I(0) = \frac{A_1}{Z_0} - \frac{A_2}{Z_0}$$

$$A_1 + A_2 = U_g - Z_1 \left(\frac{A_1}{Z_0} - \frac{A_2}{Z_0} \right)$$

$$A_1 \left(\frac{Z_0 + Z_1}{Z_0} \right) + A_2 \left(\frac{Z_0 - Z_1}{Z_0} \right) = U_g$$

$$A_1 - \Gamma_2 \frac{Z_1 - Z_0}{Z_0 + Z_1} = U_g \frac{Z_0}{Z_0 + Z_1}$$

koeficijent refleksije
na ulazu Γ_1

Vrijedi:

$$A_1 - \Gamma_1 A_2 = U_g \frac{Z_0}{Z_0 + Z_1}$$

$$A_2 = A_1 \Gamma_2 e^{-2\gamma l}$$

$$A_1 - A_1 \Gamma_1 \Gamma_2 e^{-2\gamma l} = U_g \frac{Z_0}{Z_0 + Z_1}$$

$$A_1 = U_g \frac{Z_0}{Z_0 + Z_1} \frac{1}{1 - \Gamma_1 \Gamma_2 e^{-2\gamma l}}$$

$$A_2 = U_g \frac{Z_0}{Z_0 + Z_1} \cdot \frac{\Gamma_2 e^{-2\gamma l}}{1 - \Gamma_1 \Gamma_2 e^{-2\gamma l}}$$